


Include units in your answers where appropriate.

1. Circle T (true) or F (false) for each of these Boolean equations.



- (a). ☒ T ☐ F A mesh is a loop with other loops inside it.  
 (b). ☒ T ☐ F A voltage source with series R transforms to a current source with R in parallel.  
 (c). ☒ T ☐ F The Thévenin equivalent voltage  $V_{TH}$  is the open-circuit voltage.  
 (d). ☒ T ☐ F Superposition sums the individual responses due to each independent source.  
 (e). ☐ T ☒ F Ideal op amps operate in saturation.
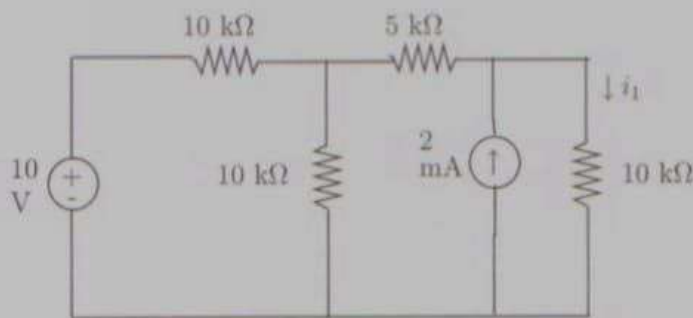
## 2. Source Transformations:


Using source transformation, find the current  $i_1$  flowing through the  $10\text{ k}\Omega$  resistor in the circuit given below. Draw a small sketch of each transformation you make.


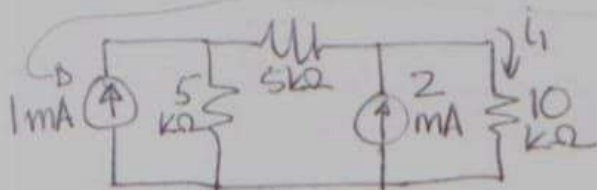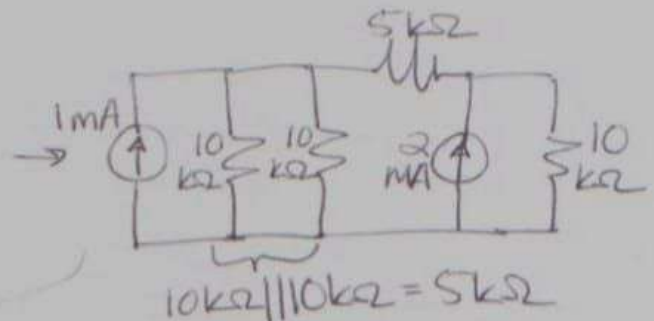
$$I_{S_1} = \frac{10\text{ V}}{10\text{ k}\Omega} = 1\text{ mA}$$



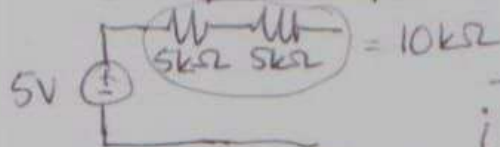
$$V_{S_2} = I_{S_1} (5\text{ k}\Omega) = 1\text{ mA} (5\text{ k}\Omega) = 5\text{ V}$$



$$I_{S_3} = \frac{V_{S_2}}{10\text{ k}\Omega} = \frac{5\text{ V}}{10\text{ k}\Omega} = 0.5\text{ mA}$$

• Current sources in || add:  
 $0.5\text{ mA} + 2\text{ mA} = 2.5\text{ mA}$

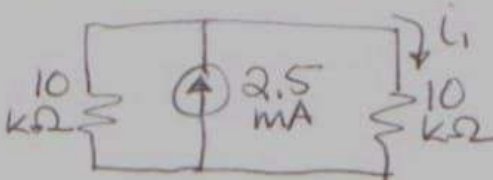


$$i_1 = 1.25\text{ mA}$$

Use Current Divider:


$$i_1 = \frac{I_s (10\text{ k}\Omega)}{10\text{ k}\Omega + 10\text{ k}\Omega} = \frac{2.5\text{ mA} (10\text{ k}\Omega)}{20\text{ k}\Omega} = 1.25\text{ mA}$$

**3. Thévenin's Equivalent Circuit with Independent Sources:**

Given the resistive circuit below:

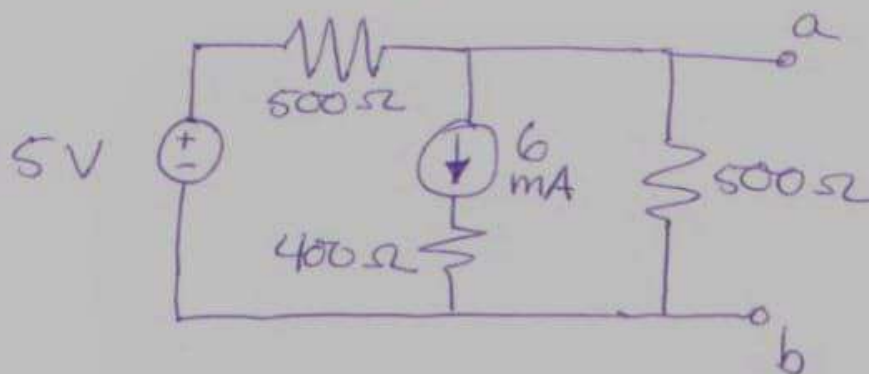

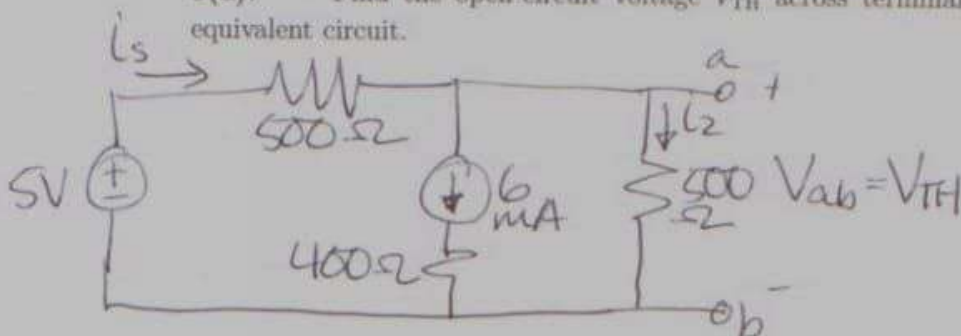3(a). Find the open-circuit voltage  $V_{TH}$  across terminals a and b of the Thévenin equivalent circuit.



• Ohm's Law:  $V_{TH} = 500 i_2$  or  $i_2 = V_{TH}/500$

• KVL:  $-5V + 500 \cdot i_s + V_{TH} = 0$

$i_s = (5 - V_{TH})/500$

• KCL at node a:  $-i_s + 6mA + i_2 = 0$

Plug in values for  $i_s + i_2$ :


$-(5 - V_{TH})/500 + 6mA + V_{TH}/500 = 0$

$V_{TH} \left( \frac{1}{500} + \frac{1}{500} \right) = \frac{5}{500} - 6mA = (10 - 6)mA = 4mA$

$V_{TH} = 4mA \left( \frac{500}{2} \Omega \right) = 1000mV = 1V$

$V_{TH} = 1V$

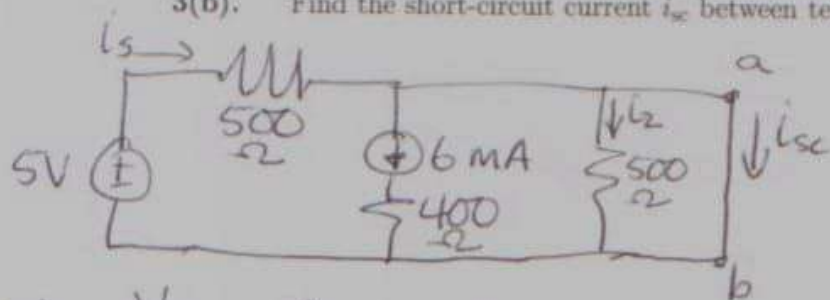3(b). Find the short-circuit current  $i_{sc}$  between terminals a and b of the circuit.



$V_{ab} = 0$  (only a wire connecting nodes a+b; no voltage drop btw a+b)

$$i_2 = \frac{V_{ab}}{500} = \frac{0}{500} = 0 \text{ A}$$

$$\text{KVL: } -5 + 500i_s + V_{ab} = 0; \quad i_s = 5/500 \text{ A} = 10 \text{ mA}$$

Node A:

$$\text{KCL: } -i_s + 6 \text{ mA} + i_2 + i_{sc} = 0$$

$$i_{sc} = i_s - 6 \text{ mA} = (10 - 6) \text{ mA} = 4 \text{ mA}$$

$$i_{sc} = 4 \text{ mA}$$


3(c). Find the Thévenin resistance  $R_{TH}$  of the Thévenin equivalent circuit, using your results for parts 3(a) and 3(b) above.

$$R_{TH} = V_{TH} / i_{sc} = \frac{1 \text{ V}}{4 \text{ mA}} = 250 \Omega$$

$$R_{TH} = 250 \Omega$$

- 3(d). Find the Thévenin resistance  $R_{TH}$  of the Thévenin equivalent circuit by finding the equivalent resistance  $R_{eq}$  with respect to terminals a and b when all independent sources are removed (deactivated).

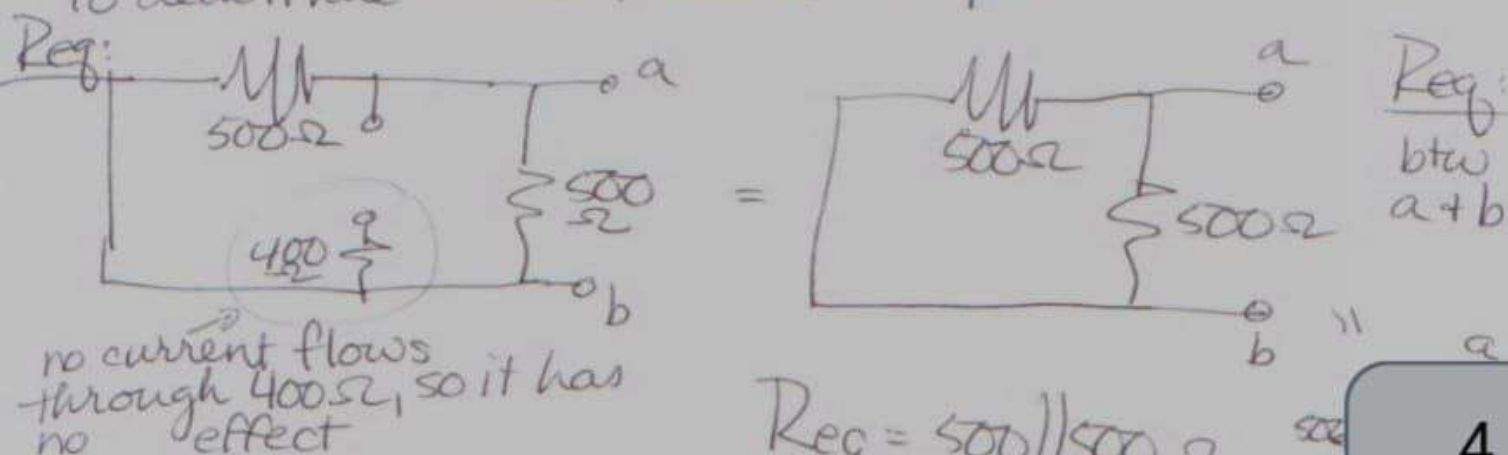To deactivate voltage source  $\rightarrow$  short circuit  
 To deactivate current source  $\rightarrow$  open circuit



$$\begin{aligned}
 R_{eq} &= 500 \parallel 500 \Omega \\
 &= \frac{500(500)}{500 + 500} \Omega \\
 &= \frac{500(500)}{2(500)} = 250 \Omega
 \end{aligned}$$


$$R_{TH} = 250 \Omega$$

- 3(e). Are your results for  $R_{TH}$  in parts 3(c) and 3(d) the same?  
 (circle one): ☒ Yes ☐ No

Should they be the same?

- (circle one): ☒ Yes ☐ No

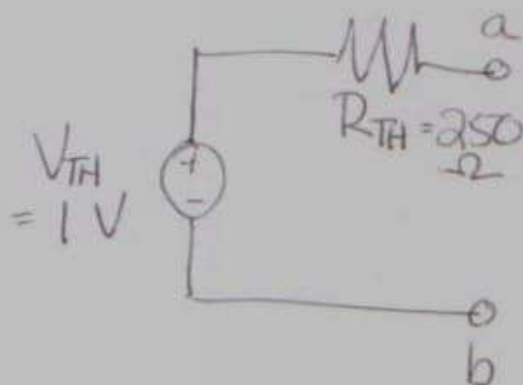- 3(f). Draw your Thévenin equivalent circuit below.






**5. Norton's Equivalent Circuit:**

5(a). Find the Norton equivalent circuit for the circuit given in problem 4. What is the Norton current source,  $I_N$ ?

$$I_N = V_{TH}/R_{TH} = \frac{1\text{ V}}{250\ \Omega} = 4\text{ mA}$$

$$I_N = 4\text{ mA}$$

5(b). Draw your Norton equivalent circuit below.

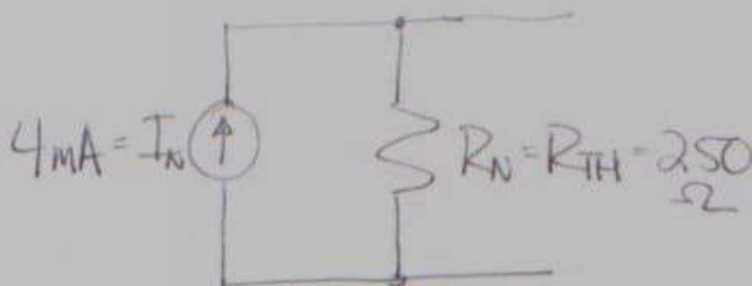**6. Maximum Power Transfer:**

6(a). Using the circuit in problem 4, what value of load resistance  $R_L$  will provide the maximum power transferred to the load  $R_L$ ? You don't have to prove what value will provide maximum power, just use the appropriate value of  $R_L$  that does provide maximum power.

$$R_L = R_{TH} = 250\ \Omega$$

$$R_L = 250\ \Omega$$


6(b). Using the value of  $R_L$  obtained above, find the power  $P_L$  transferred to (or absorbed by) the load  $R_L$ .

(Voltage Divider)


$$P_L = \frac{V_L^2}{R_L} = \frac{V_L^2}{R_{TH}}; V_L = \frac{V_{TH} R_L}{R_{TH} + R_L} = \frac{V_{TH} R_{TH}}{2 R_{TH}} = \frac{V_{TH}}{2}$$

$$P_L = \frac{(V_{TH}/2)^2}{R_{TH}} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{1}{4(250)} = \frac{1}{1000} = 1\text{ mW}$$

$$P_L = 1\text{ mW}$$

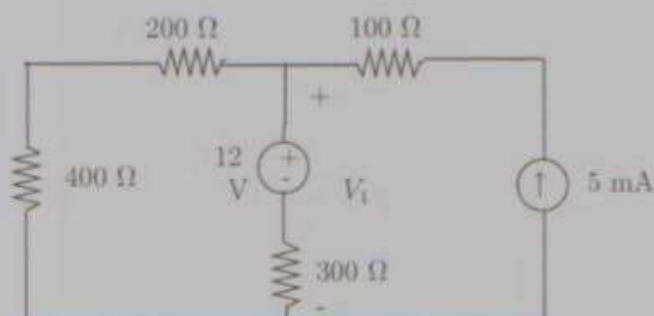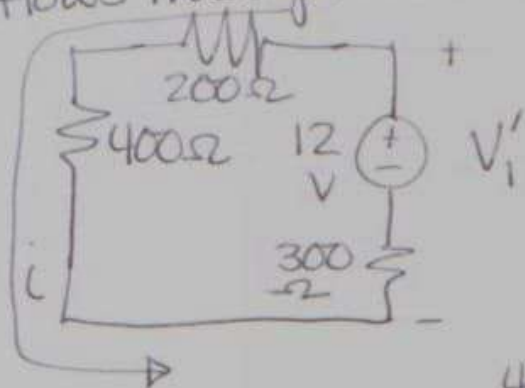
**7. Superposition:**Use superposition on the circuit below to find the voltage  $V_i$ .7(a). Find the voltage  $V_i'$  due to the 12 V voltage source alone.

• Deactivate current source: becomes open circuit; no current flows through  $100\Omega$  R so can ignore it



• Current  $i$  flows from + to - terminal of 12 V source

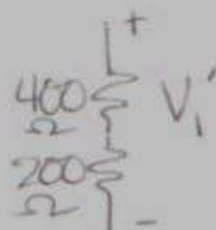•  $V_i' =$  voltage across 12 V source  $- 300\Omega \cdot i$   
 $=$  voltage across  $400 + 200\Omega$  resistors



• Use voltage divider:

$$V_s = 12V$$

$$V_i' = V_s \frac{400 + 200}{400 + 200 + 300}$$

$$= \frac{V_s (600)}{900} = \frac{12(2)}{3} = 8V$$

$$V_i' = 8V$$

6

or use KVL

$$\bullet -i(400 + 200) + V_i' = 0; V_i' = 600i$$

$$\bullet -i(400 + 200) + 12 - i(300) = 0; 900i = 12; i = 12/900$$

$$V_i' = 600 \left( \frac{12}{900} \right) = 8V \quad (\text{same eqn as voltage divider})$$