

VOLTAGE (or) POTENTIAL :-

→ The Amount of work done to bring a unit positive charge from ∞ to a point is known as absolute potential of that point. We are interested in potential difference (Voltage) between two points.

→ If the Energy required to move a charge of Q coulombs from point A to point B is W Joules, the Voltage V between A and B is given as

$$V = \frac{W}{Q}$$

→ The unit of Voltage is Volt. $1 \text{ Volt} = 1 \text{ Joule/Coulomb}$

Energy :-

→ Capacity to do work is called as Energy. The unit of Energy is Joules.

→ If current is entering at +ve terminal of an element, then the element is absorbing the energy. Vice-versa.

POWER :-



→ Consider an element having a voltage V across it. A small change in charge Δq is moved through element from the positive terminal to the negative terminal in time Δt . The Energy ΔW absorbed by the element in this process is given as $\Delta W = V \Delta q$.

$$\text{i.e. } \frac{\Delta W}{\Delta t} = V \cdot \frac{\Delta q}{\Delta t}$$

$$\Rightarrow \frac{dW}{dt} = \frac{dq}{dt} \cdot V = Vi = P$$

→ The Rate of doing work is known as power.

$$P = VI$$

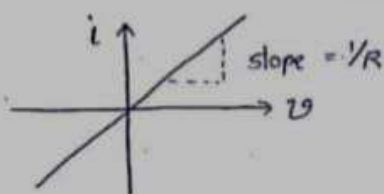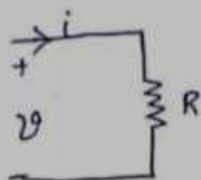

OHM'S LAW in graphical form.

Applications of OHM'S LAW:-

- i) $V = IR$, $P = VI = I^2 R = V^2/R$. When two quantities are known, we can easily calculate the third quantity by using ohm's law.

Limitation of OHM'S LAW:-

1. This law can't be applied unilateral network. Eg: Network having Diodes etc.
2. ohm's law also not applicable to non-linear elements. Eg. Diode, transistor etc.

POWER AND ENERGY IN RESISTOR:-

→ From ohm's law, $V = IR$.

$$\text{Power} = P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V \cdot I \text{ watt}$$

$$\Rightarrow \begin{aligned} P &= VI \text{ watt} \\ &= I^2 R \text{ watt} \\ &= V^2/R \text{ watt.} \end{aligned}$$

→ Energy (I will denote with E or W). is given by

$$P = \frac{dw}{dt} \text{ where } w \text{ is workdone (Energy).}$$

$$\Rightarrow P \cdot dt = dw$$

$$\Rightarrow \int P \cdot dt = \int dw$$

$$\Rightarrow W \text{ or } E = \int P \cdot dt \text{ J (or) Joule.}$$

$$\therefore E = \int VI \cdot dt = \int I^2 R \cdot dt = \int \frac{V^2}{R} \cdot dt$$

POWER AND ENERGY IN CAPACITOR :-

(4)

→ The property of material which stores energy in an electric field is known as Capacitance. (C). units are Farad (F)

→ A Capacitance (C) satisfies a Relation,

$$i = C \cdot \frac{dv}{dt}$$

→ power in a Capacitor = $p = v \cdot i$

$$\Rightarrow p = \frac{dv}{dt} \cdot C \cdot v$$

$$\Rightarrow \boxed{p = C \cdot v \cdot \frac{dv}{dt}} \text{ Watt.}$$

→ Energy in a Capacitor = $E = \int p \cdot dt$

$$= \int C \cdot v \cdot \frac{dv}{dt} \cdot dt$$

$$\Rightarrow \boxed{E = \frac{1}{2} C v^2} \text{ Joule}$$

POWER AND ENERGY IN INDUCTOR :-

→ The property of material which stores energy in Magnetic field is known as Inductance. (L). units are Henry (H)

→ An Inductor satisfies a Relation,

$$v = L \cdot \frac{di}{dt}$$

→ power in an Inductor = $p = v \cdot i$

$$= L \cdot \frac{di}{dt} \cdot i$$

$$\Rightarrow \boxed{p = L i \frac{di}{dt}} \text{ Watt}$$

→ Energy in an Inductor = $E = \int p \cdot dt = \int L i \frac{di}{dt} \cdot dt$

$$\Rightarrow \boxed{E = \frac{1}{2} L i^2} \text{ Joule.}$$



→ when Three Capacitors are in parallel. The Equivalent Capacitance C_{eq} is given by $C_{eq} = C_1 + C_2 + C_3$ where C_1, C_2 and C_3 are given capacitances.

→ when C_1, C_2 , and C_3 are in series. Then

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


6

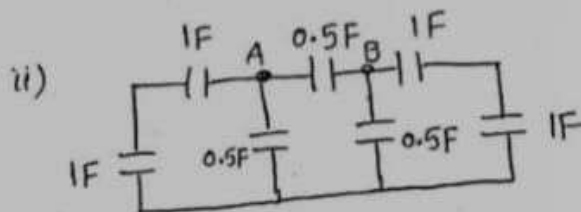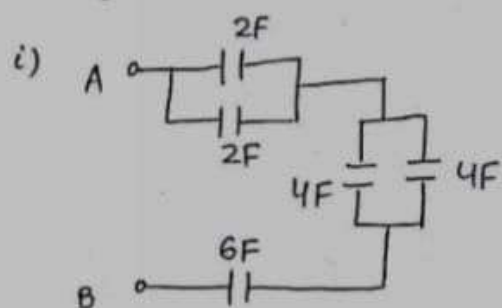Q. Calculate Equivalent Capacitance between A and B terminals in the following Circuits.




Sol:- i)
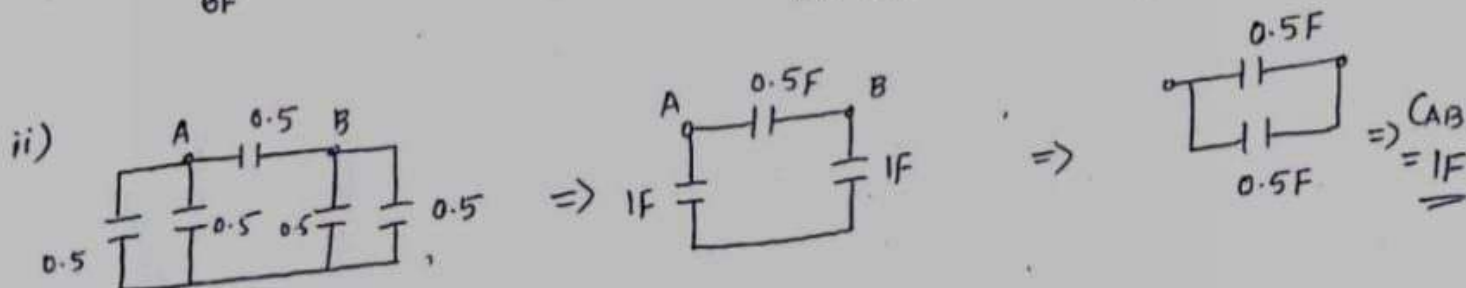
$$\Rightarrow C_{AB} = \frac{(4F) \left[\frac{2 \times 4}{2+4} \right]}{4 + \left[\frac{2 \times 4}{2+4} \right]} = \frac{4 \times \frac{8}{6}}{4 + \frac{8}{6}} = 1.84F$$



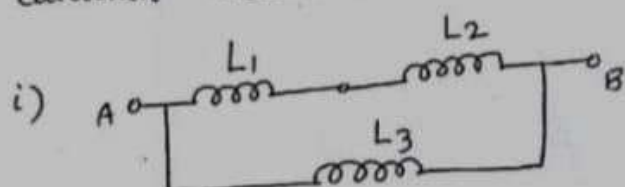Q. Calculate Equivalent inductance b/w A and B terminals.



ii) If $L_1 = 2H$, $L_2 = 4H$, $L_3 = 6H$.
 $L_{AB} = ?$

Sol:- i)


$$L_{AB} = \frac{L_3(L_1 + L_2)}{L_3 + L_1 + L_2}$$

ii)


$$L_{AB} = \frac{6(4+2)}{6+4+2} = 3H$$

STAR TO DELTA & DELTA TO STAR CONVERSION:-

(7)

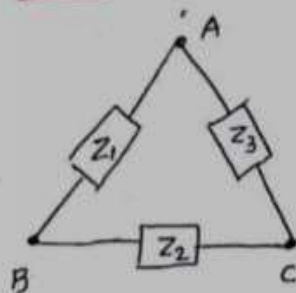

Delta connection

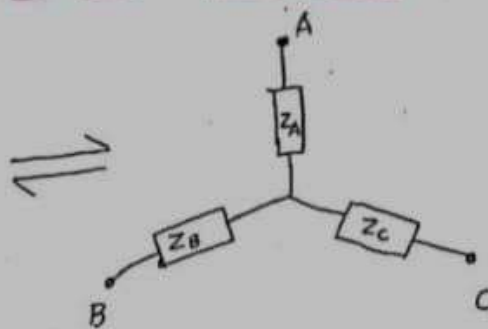

Star connection.

7

→ Delta to Star conversion:- (Assume above values of impedances)

$$Z_A = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_B = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_C = \frac{Z_3 Z_2}{Z_1 + Z_2 + Z_3}$$

→ STAR TO DELTA CONVERSION:-

$$Z_1 = Z_A + Z_B + \frac{Z_A Z_B}{Z_C}$$

$$Z_2 = Z_B + Z_C + \frac{Z_B Z_C}{Z_A}$$

$$Z_3 = Z_A + Z_C + \frac{Z_A Z_C}{Z_B}$$

→ In Case Resistor,

i) STAR TO DELTA:

$$R_1 = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_2 = R_B + R_C + \frac{R_B R_C}{R_A}$$

$$R_3 = R_A + R_C + \frac{R_A R_C}{R_B}$$

ii) DELTA TO STAR:-

$$R_A = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

→ In Case of Capacitor,

i) STAR TO DELTA:-


$$\frac{1}{j\omega C_1} = \frac{1}{j\omega} \left[\frac{1}{C_A} + \frac{1}{C_B} + \frac{C_C}{C_A C_B} \right]$$

$$\Rightarrow \frac{1}{C_1} = \frac{1}{C_A} + \frac{1}{C_B} + \frac{C_C}{C_A C_B}$$

DELTA TO STAR

$$\frac{1}{C_A} = \frac{\frac{1}{C_1} \cdot \frac{1}{C_3}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

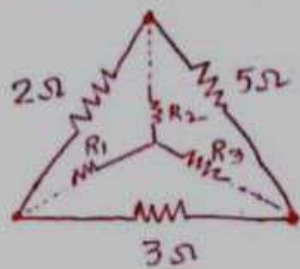- Q. If Delta connection is converted into star equivalent. Then calculate R_1, R_2, R_3 values in the following network.




Sol:-

$$R_1 = \frac{2(3)}{2+3+5} = \frac{6}{10} = 0.6\Omega$$

$$R_2 = \frac{2(5)}{2+3+5} = \frac{10}{10} = 1\Omega$$




$$R_3 = \frac{3(5)}{2+3+5} = \frac{15}{10} = 1.5\Omega$$

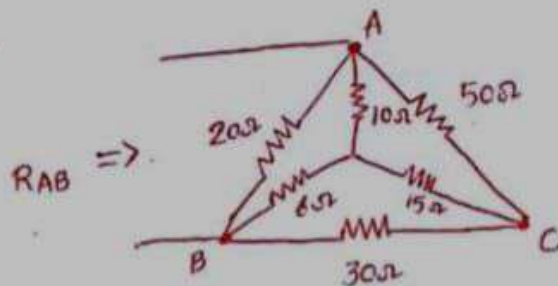- Q. Find Equivalent Resistance between A and B terminals in the following network.




Sol:-

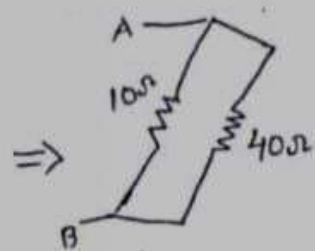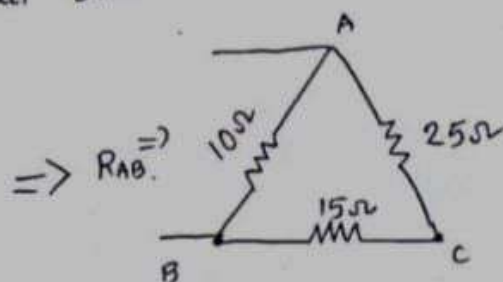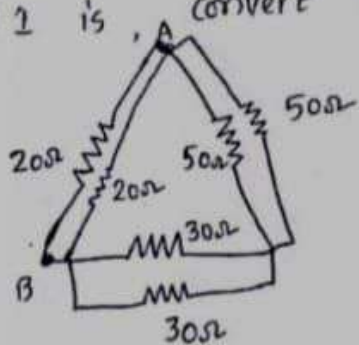Step 1 is, convert internal star into Delta network.



$$\therefore R_{AB} = \frac{10(40)}{10+40} = \frac{400}{50} = 8\Omega$$

Hint:- convert

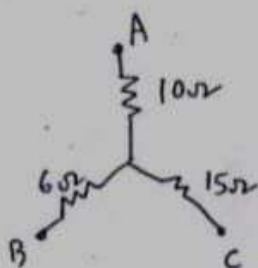

$$\Rightarrow \begin{aligned} 50\Omega &= 10 + 15 + \frac{10(15)}{6} \\ &= 6 + 15 + \frac{15(6)}{10} \end{aligned}$$